

Transmission line model of cavity with coupler


C.Y. Tan
30 Sep 2014

Goal

- Create semi-analytic model to see what's going on.
 - Voltage profile along the cavity.
 - How to add coupler.
 - What the reflection coefficient is at the coupler.
 - Does adding a “neck” help with impedance matching or voltage shaping? ← not done yet!
- **Caveat Emptor! Results discussed here are all PRELIMINARY probably not right!**
 - **Subject to change without notice, apologies or regret!!!!**

Transmission line model

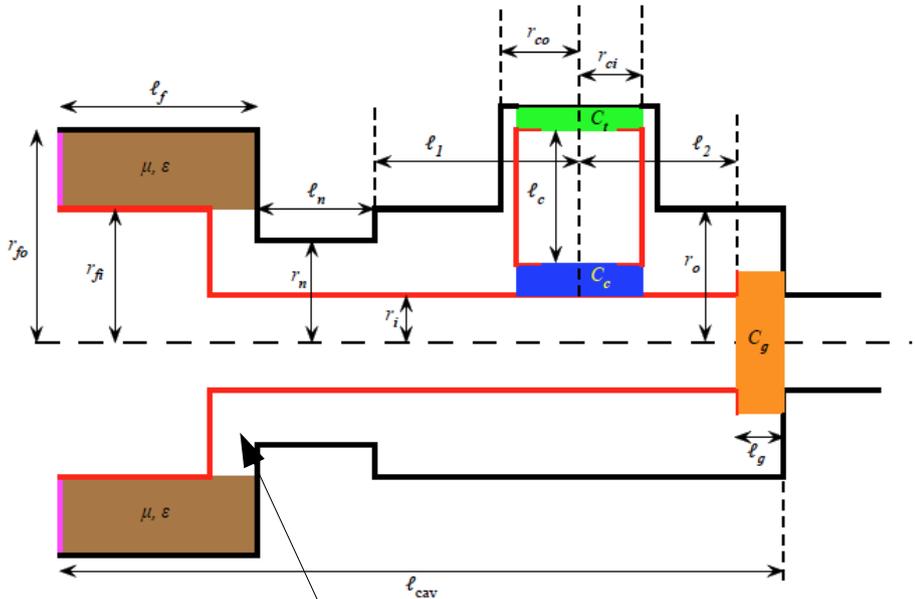Too complicated! So work with even simpler model



Neglecting this part

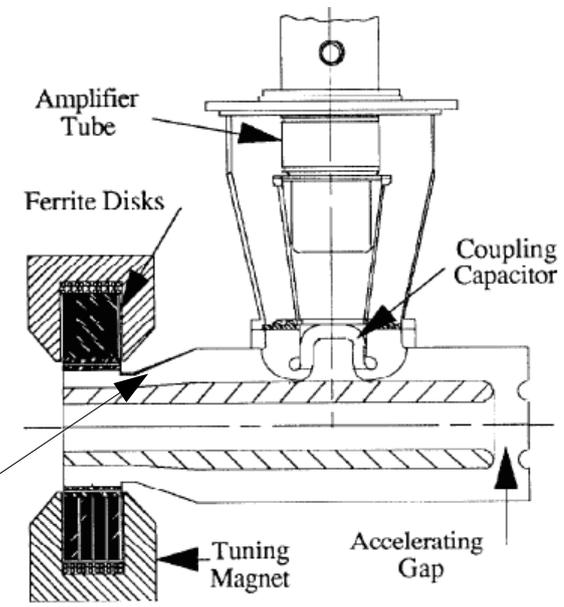
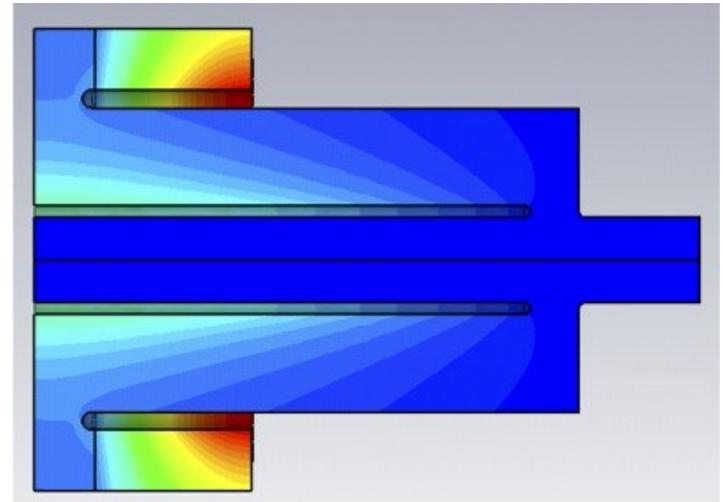
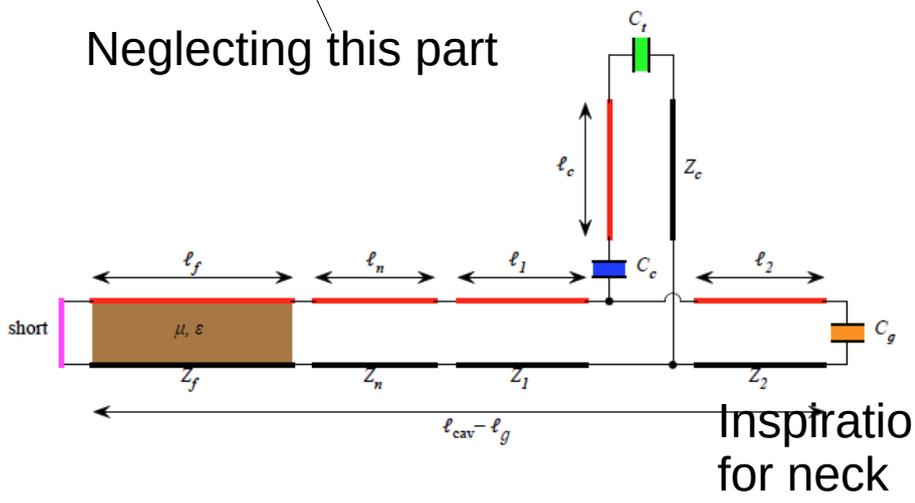


Fig. 1. The Proposed LEB Cavity

Simple garnet loaded cavity


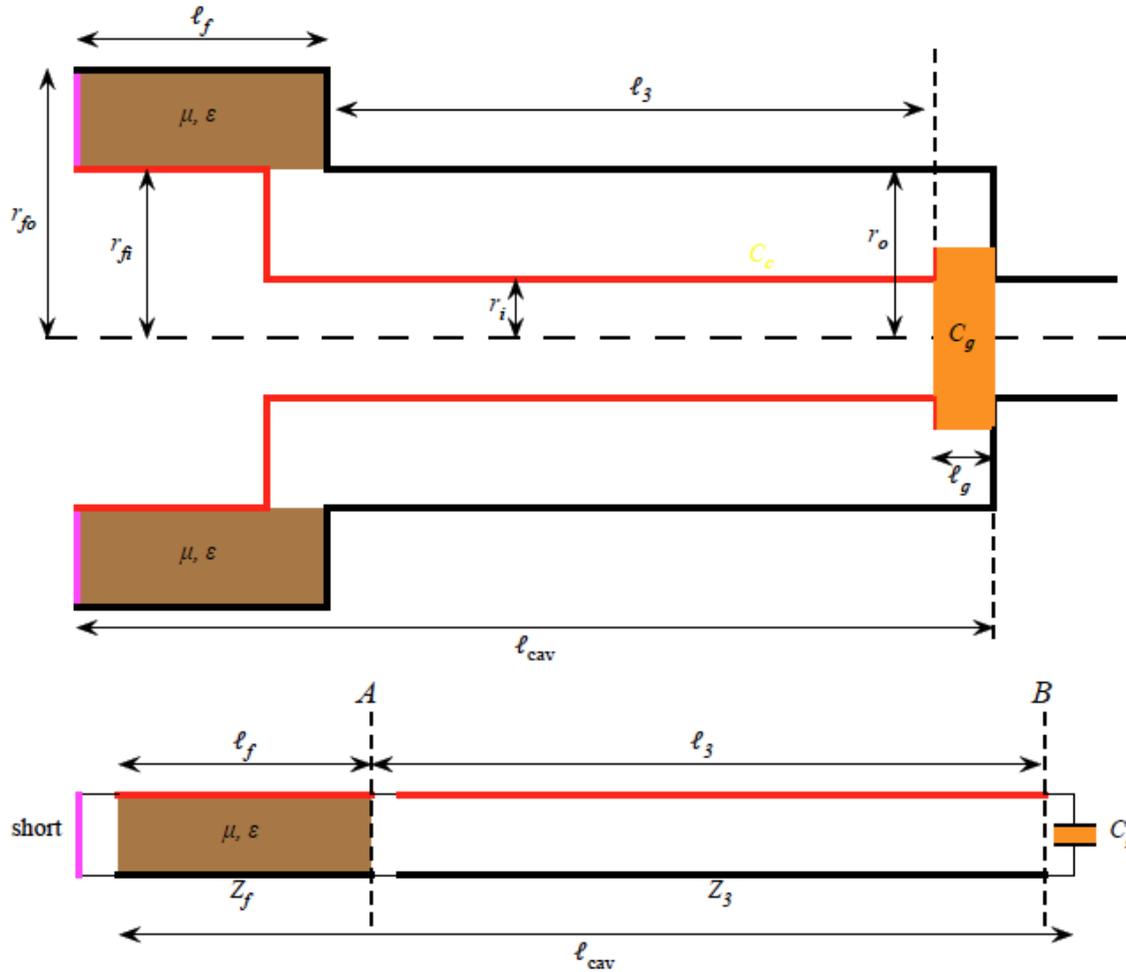


TABLE I. Equivalent circuit parameters


Part	Parameter	Value	Units	Description
	r_i	0.035	m	radius of the beam tube.
	ℓ_f	0.195	m	length of the garnet.
	ℓ_g	0.04	m	length of the gap.
z_f		17.17	Ω	characteristic impedance of the garnet.
	μ_r	3.5		relative permeability of garnet at 76 MHz.
	ϵ_r	14		relative permeability of garnet.
	ℓ_f	0.195	m	length of the garnet.
	r_{fo}	0.195	m	outer radius of the garnet
	r_{fi}	0.110	m	inner radius of the garnet
z_n		tbd[2]	Ω	characteristic impedance of the neck.
	ℓ_n	tbd	m	length of the neck.
	r_n	tbd	m	outer radius of the neck
$z_{1,2}$		62.9	Ω	characteristic impedance of the non-ferrite part.
	$\ell_{1,2}$	0.25	m	length of transmission line 1.
	r_o	0.10	m	outer radius of transmission line 1.
z_3		62.9	Ω	characteristic impedance of the non-ferrite part.
	ℓ_3	0.5	m	length of transmission line 1.
	r_o	0.10	m	outer radius of transmission line 1.
z_c		40.6[3]	Ω	characteristic impedance of the coupler.
	ℓ_c	tbd	m	length of the coupler.
	r_{co}	0.25 ^A	m	outer radius of the coupler.
	r_{ci}	0.127 ^A	m	inner radius of the coupler.
	C_t	56	pF	tube capacitance from anode to screen.
	C_c	8	pF	coupling capacitance.
	C_g	18.76[4]	pF	gap capacitance.

Results

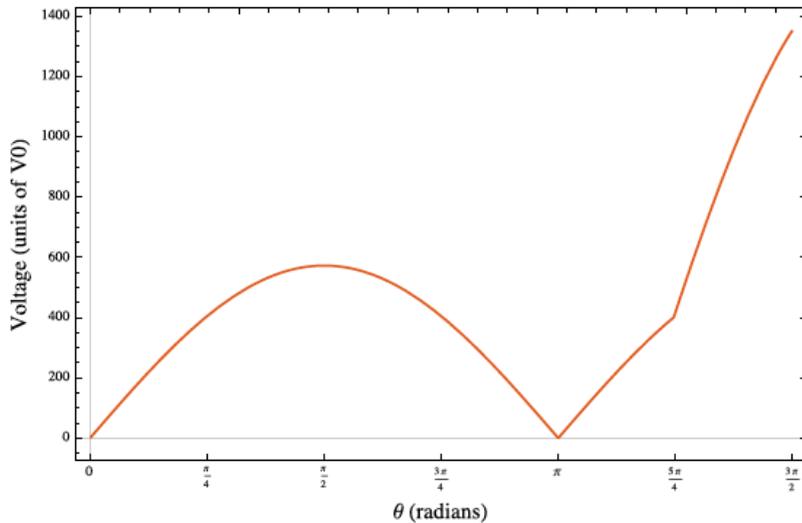Behaviour of voltage along cavity with 1 node in garnet



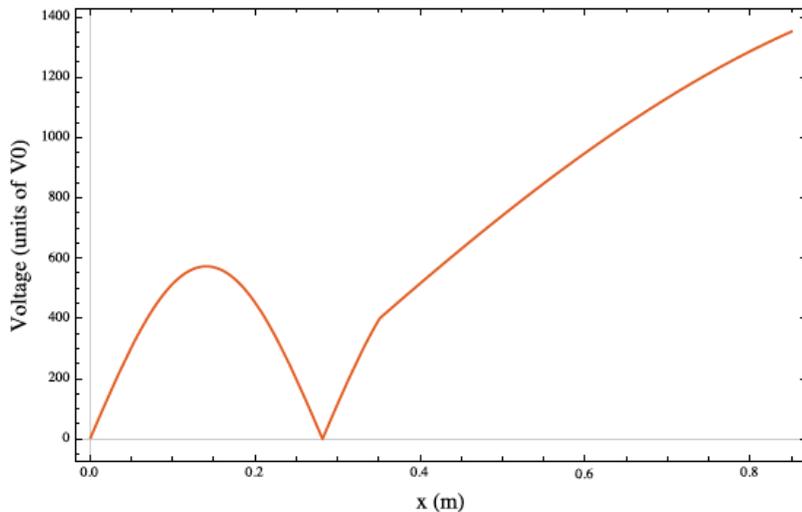Behaviour of voltage along cavity with 1 node in garnet




I force the length of the garnet+non-garnet part = $3\pi/2$ or $3\lambda/4$ and find that:

Length of garnet = 0.35 m

Length of non-garnet = 0.5 m

Gap capacitance = 18.76 pF


Getting C_g for total phase of $3\pi/2$

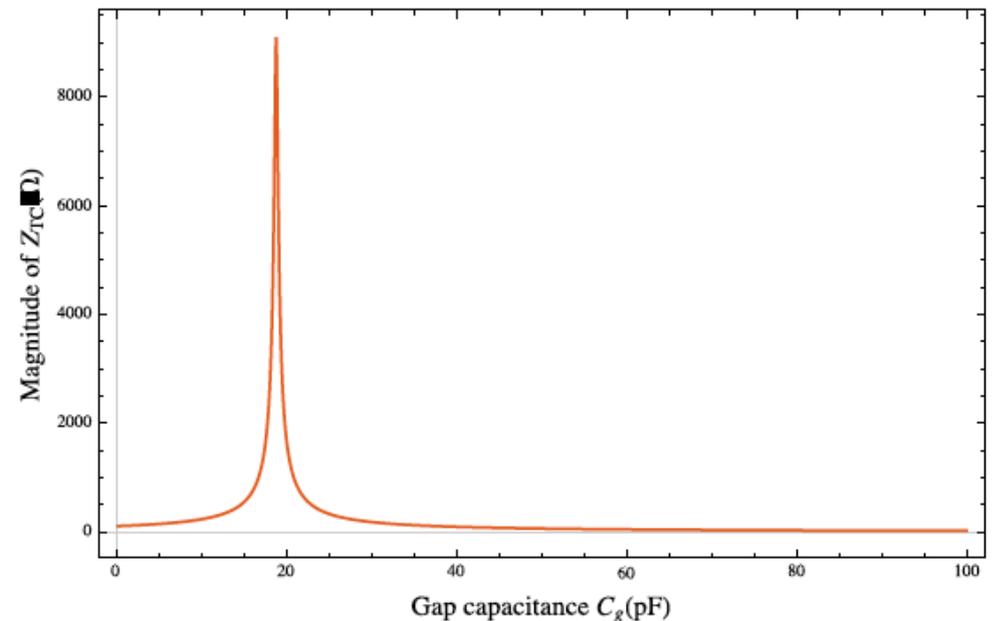

Results (cont'd)

- The cavity must be at least $3\lambda/4$ because the garnet length even in MWS has more than $\pi/2$ phase change in it.
- The cavity can be any length that we want depending on the gap capacitance.
 - I found the gap capacitance to be ~ 20 pF, expect ~ 1 pF at 76 MHz
 - Source of the problem is that $z_f = 60 \cdot \text{Sqrt}[\mu_r/\epsilon_r] \cdot \text{Log}[r_o/r_i]$ and for $\mu_r=3.5$ and $\epsilon_r=14$, $\text{Sqrt}[3.5/14] = 0.5 < 1$. And so for the same βl , the inductance is smaller ($Z = i z_0 \text{Tan}[\beta l]$ for shorted coaxial line). From the geometry of the model $z_f = 17.17\Omega$ and $z=62.9\Omega$.
 - I need to understand this! Is this a problem of the way I've set up my model?
 - There is a reduction in length, in general, from the resonant length of a shorted transmission line ($\lambda/4$ or $3\lambda/4$) due to the gap capacitor.
 - The length will affect R_s , so have to be careful. $Q = \pi/4 \cdot (z/R_s)$ where z is the characteristic impedance.

Coupler

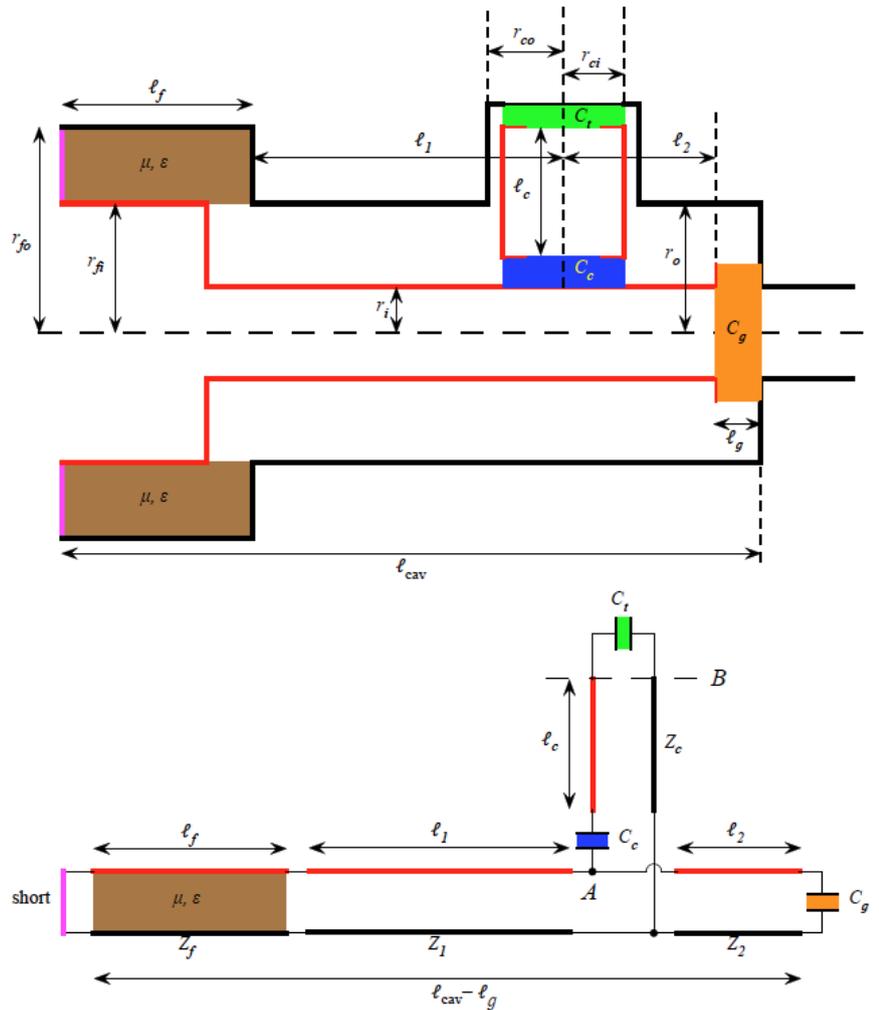



Location of coupler will be in the middle of the non-garnet part.
The centre conductor has radius 5" because of the tube anode constraints.

$$r_{ci} = 5'' = 0.127 \text{ m}, r_{co} = 0.25 \text{ m} \text{ and so } Z_c = 40.6 \Omega.$$

I chose the length of the coupler transmission line = 20 cm (\leftarrow not the right way to do this, according to Joe)

$$C_c = 8 \text{ pF}, C_t = 56 \text{ pF}.$$

Getting the resonance

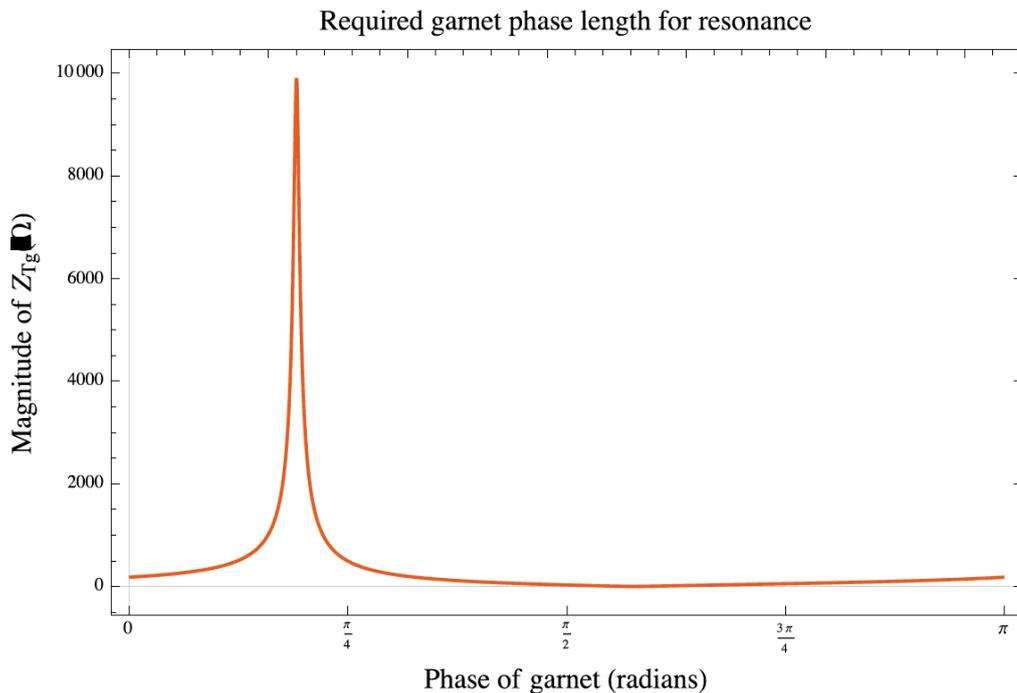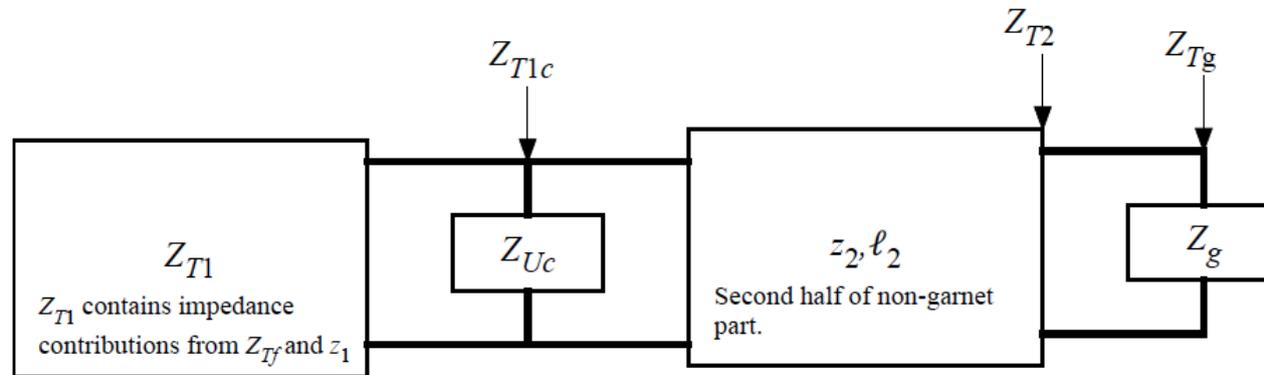




Found l_f to be a little shorter compared to without coupler.

$L_f = 0.335$ m compared to 0.35 m previously.


Reflection coefficient

Doesn't work. Too much reflection for the entire range!

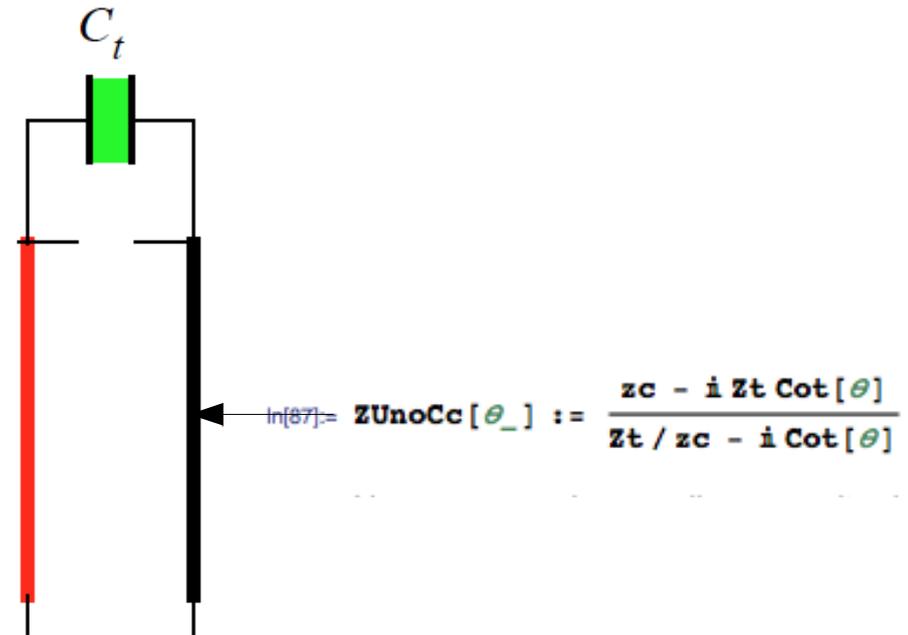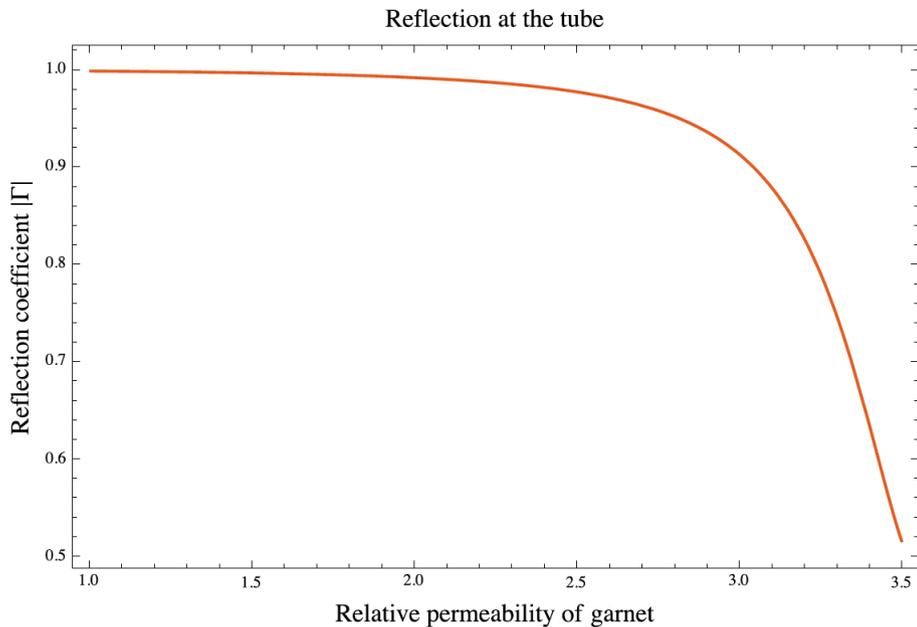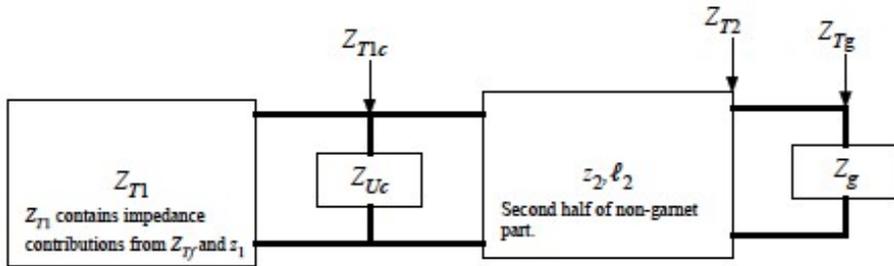Talked to Joe Dey, he suggests that I need to find the point on the line that cancels the cavity impedance.



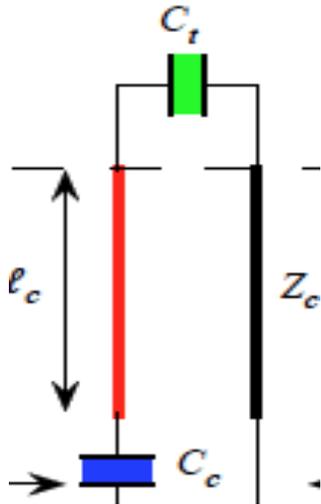Stupidly connecting coupler introduces more problems



Do the simplest case where the cavity imaginary part of the impedance is zero at the coupling point. Then, I find that

$$\text{In[93]:= FindRoot}\left[\text{Im}\left[\text{ZUnoCc}[\beta c L] + \frac{1}{i \omega 0.8 \times 10^{-12}}\right] == 0, \{L, 0.1\}\right]$$

Out[93]= {L → 3.32884}

Ooops! Coupler length is 3 m!!!!

Let's try it again with the 1000 pF coupling capacitor

$$\text{In[94]:= FindRoot}\left[\text{Im}\left[\text{ZUnoCc}[\beta c L] + \frac{1}{i \omega 0.1000 \times 10^{-12}}\right] == 0, \{L, 0.1\}\right]$$

Out[94]= {L → 0.499349}

Much more reasonable. So it is not sufficient to randomly select coupling point to be at the centre of the cavity!

Fine tune length of cavity so that at the coupling point, the imaginary part of the cavity impedance nearly cancels Z_c . This could be the trick!

Clearly more work needs to be done!

- Figure out why C_g is so large. Model problems?
- Figure out the location of the coupler so that the impedance at the coupling point mostly cancels the impedance of the coupling capacitor.
- Make sure that the entire device does resonate with the coupler added
 - Make sure that the reflection coefficient is ok.
- Perhaps Ding's HFSS? Model will give a better result.